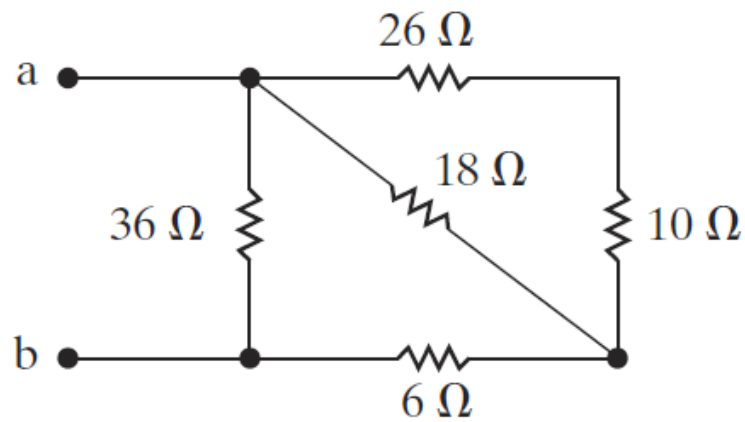



## EC1101 – Tutorial Sheet 1

For all the circuits given below, find the equivalent resistance


A




B

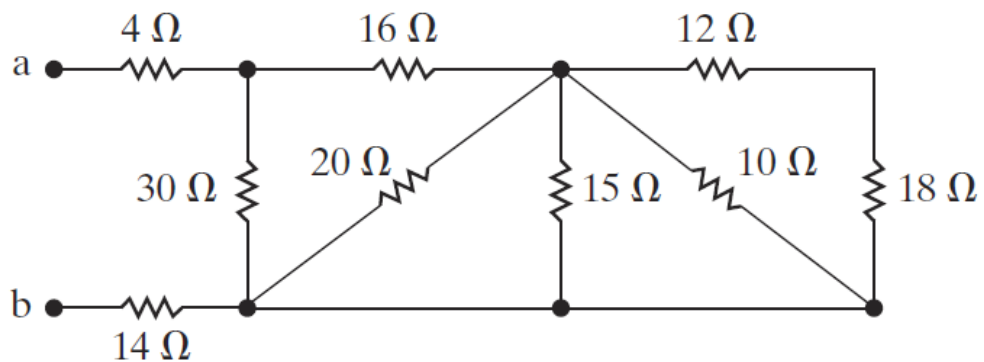


C

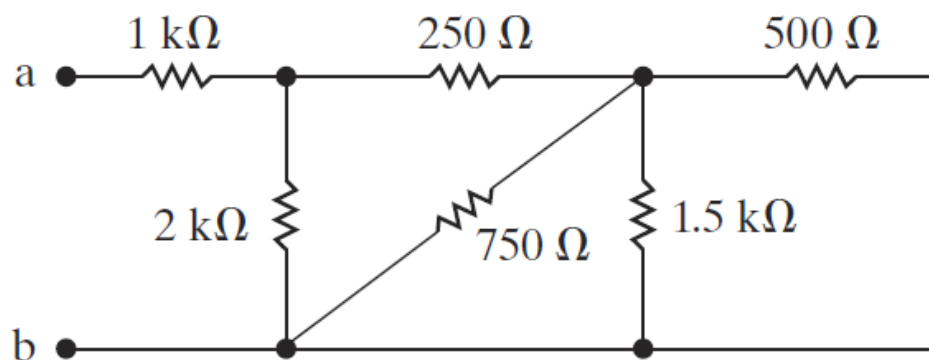

D

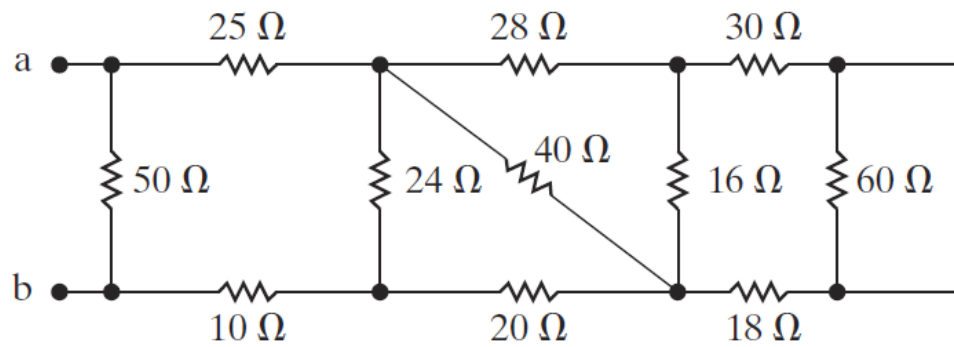


E

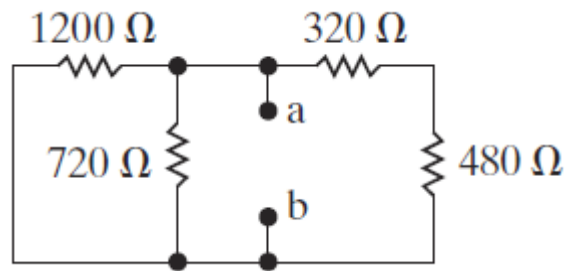


Find the equivalent resistance at a-b.

F

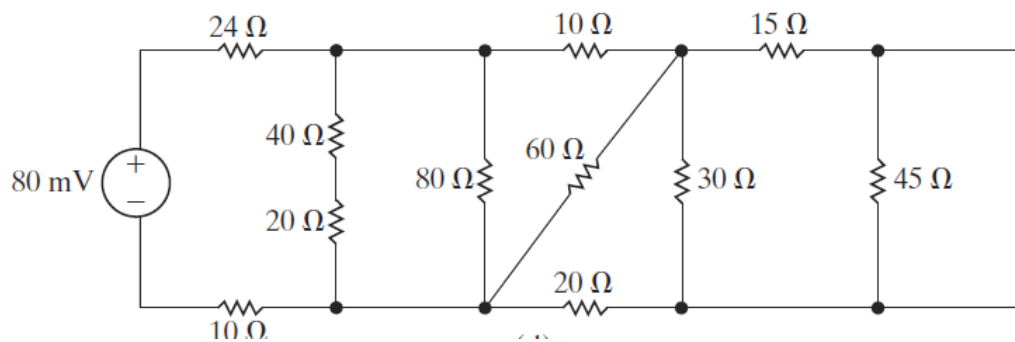

Find the equivalent resistance seen by the 80mV source

G

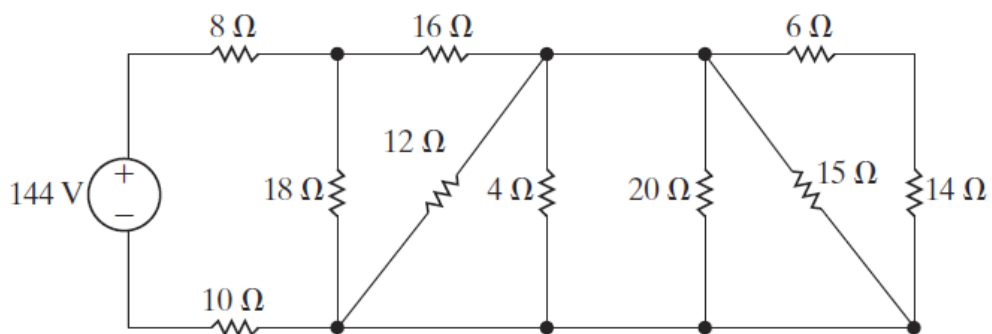

Find the equivalent resistance seen by the 144V source