
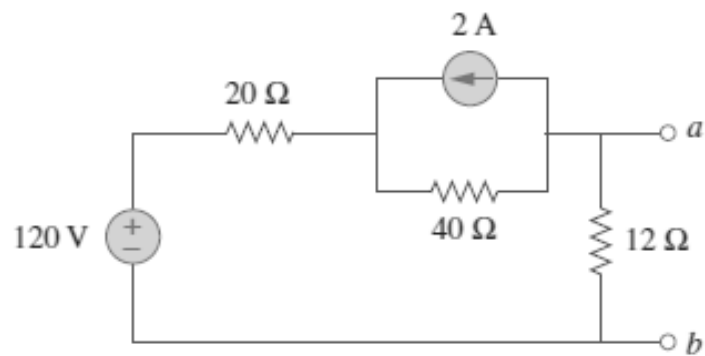


EC1101 – Tutorial Sheet 4


- 1 Find the Norton equivalent at a-b.

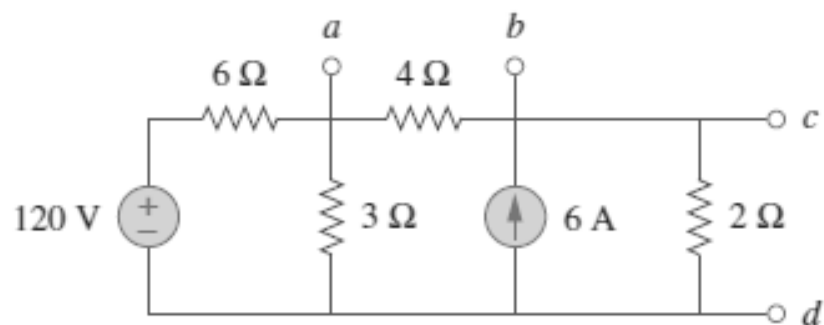


- 2 Find the Norton equivalent circuit at a-b.



3 Find v_o using Norton's theorem.

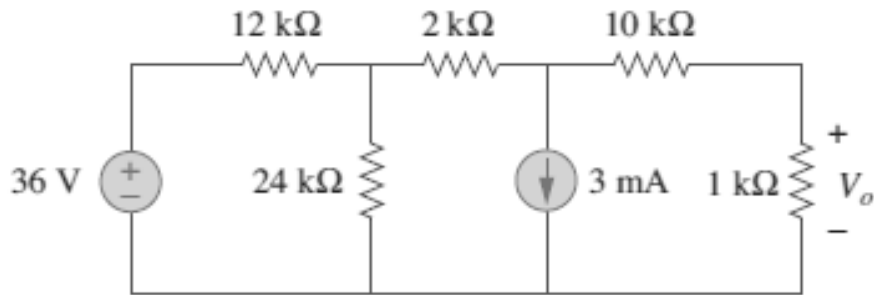

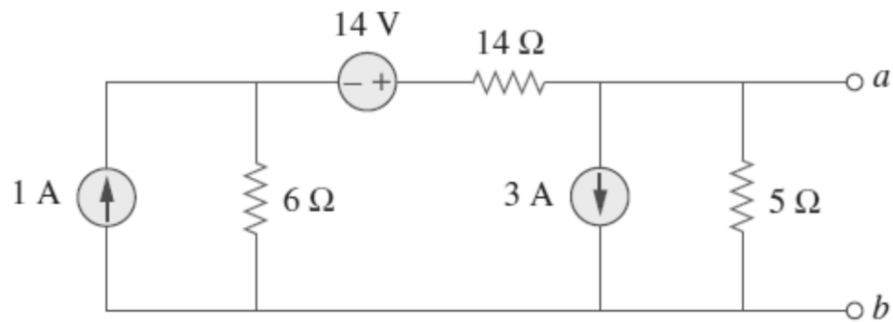4 Find the Thevenin equivalent circuit at a-b.



5 Find the Thevenin equivalent at a-b using only source transformation.

