

EC1101 - Tutorial Sheet 5

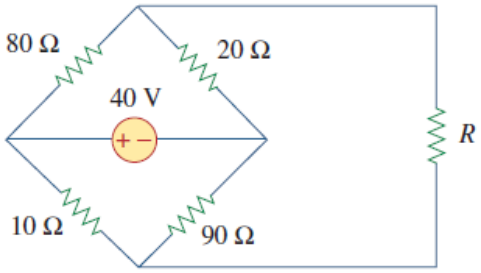
1. Find **R** for maximum power to be transferred to it and the power through it.



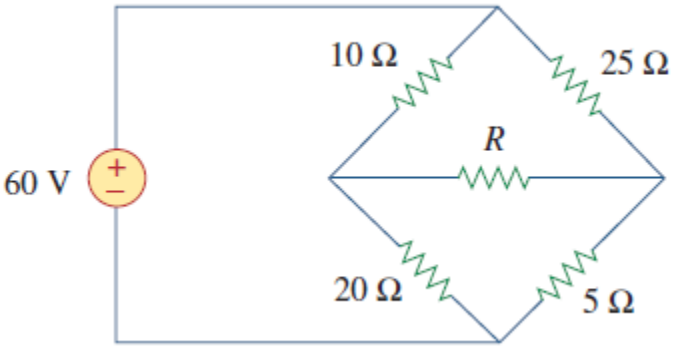2. Find R such that maximum power is transferred to it.



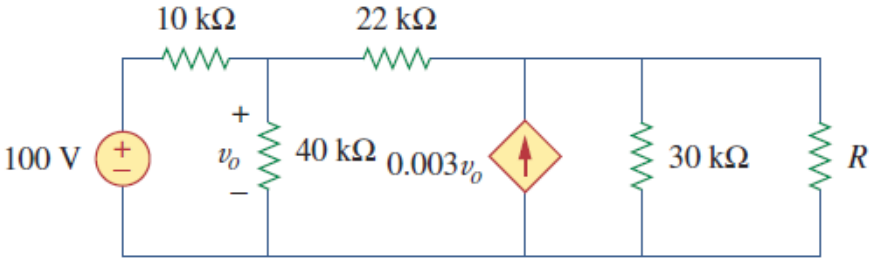3. Find the maximum power transferred to resistor R in the circuit below.



4. Determine the maximum power delivered to the variable resistor R in the circuit below.

