

EC1101 - Tutorial Sheet 7

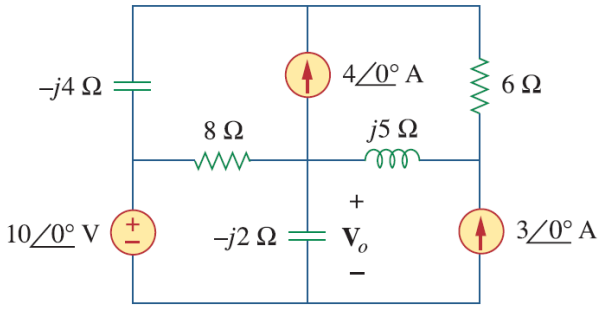
1. Find $\mathbf{V_0}$ using mesh analysis.



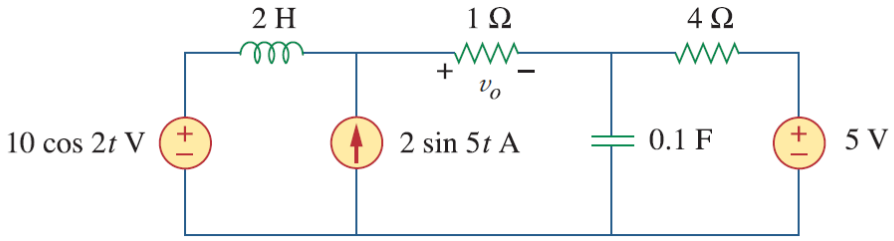
2. Find $\mathbf{v_0}$ using superposition.



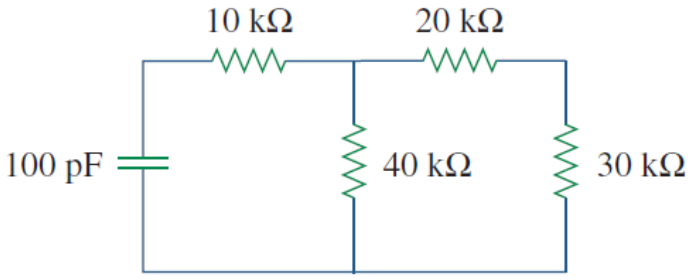3. Find the time constant for the circuit below.



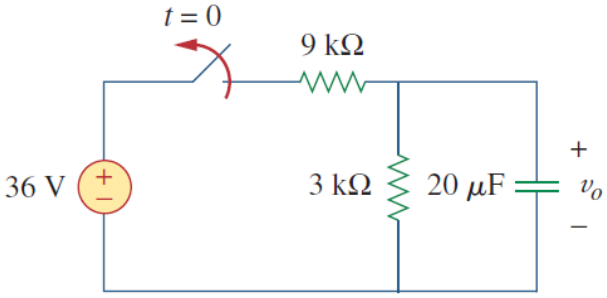4. Find $\mathbf{v_o(t)}$ for t > 0. Determine the time necessary for the capacitor voltage to decay to one-third of its value at t = 0.



5. Find $\mathbf{v_0(t)}$ if $\mathbf{i(0)}$ = 6 A and $\mathbf{v(t)}$ = 0.

