
EC1101 - Tutorial Sheet 8

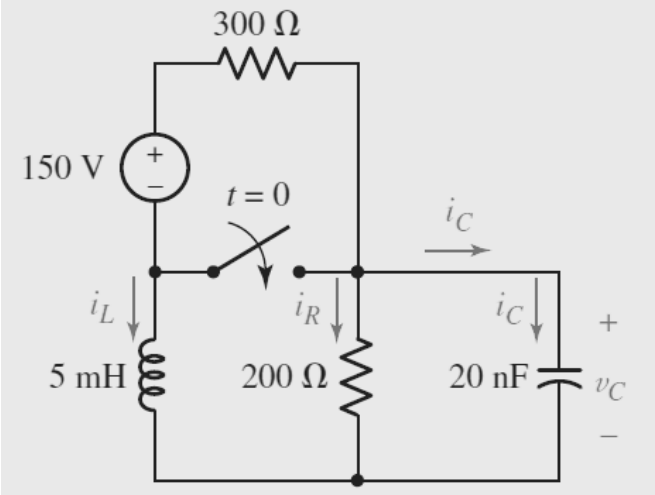1. The switch was open for a long time and closed at t=0. Find ***$v_c(t)$*** **for t>0** .



2. The switch was open for a long time and closed at t=0. Find ***i(t)*** **and** ***v(t)*** **for all t>0** .

